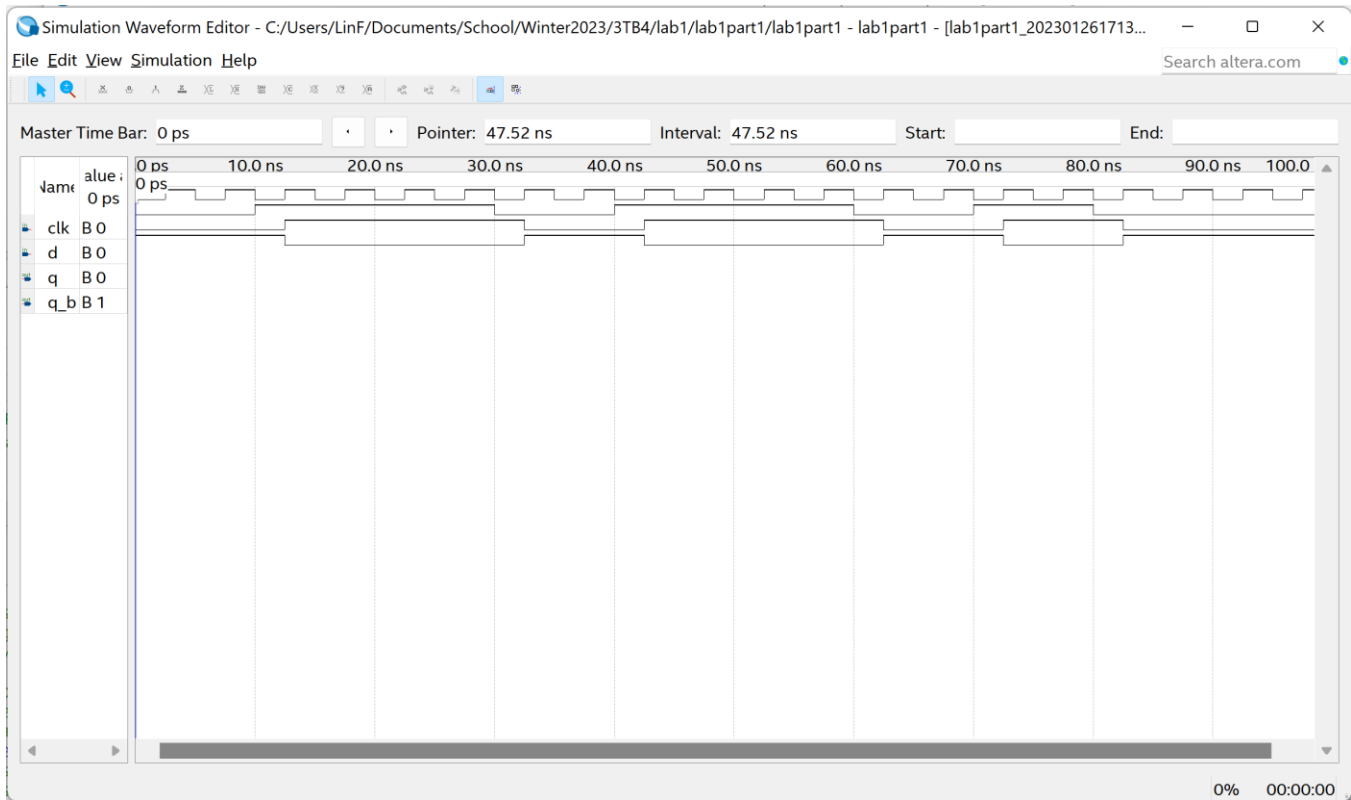


## 3TB4 Lab 1 Report


Lin Fu          ful10          400234794

Keyin Liang    liangk10      400236736


D flip-flop simulation:



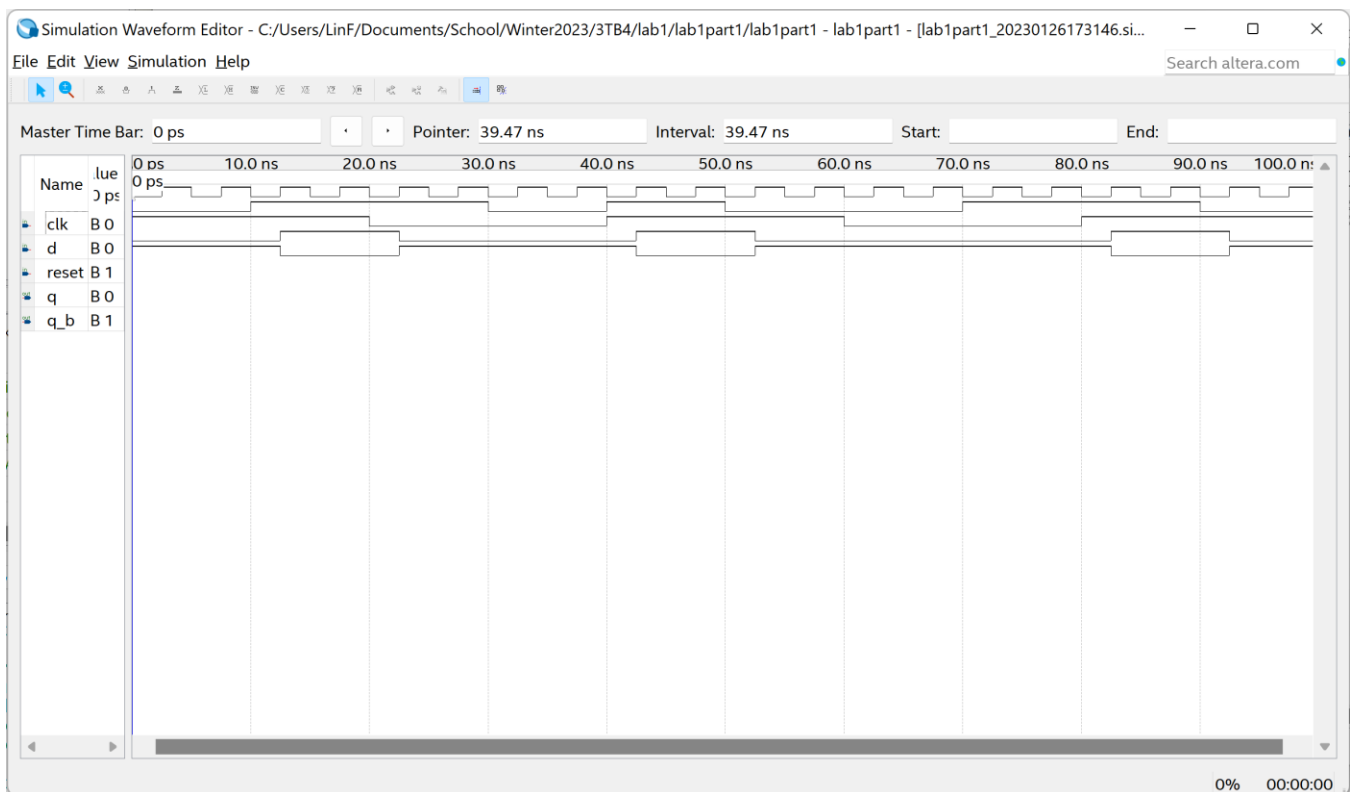
D flipflop with active low synchronous reset:



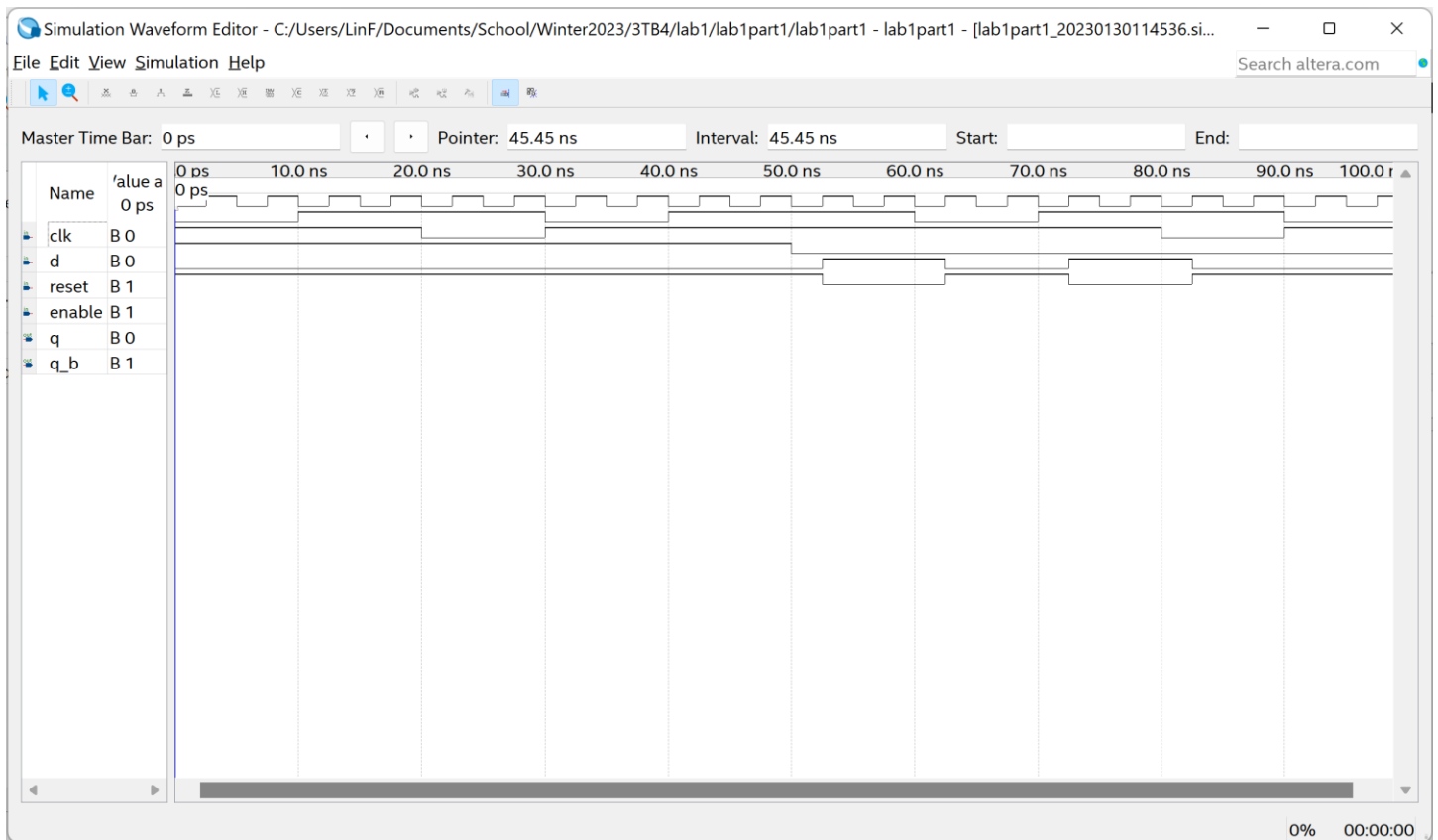
## D flipflop with active low synchronous reset and active low enable:




## D latch:

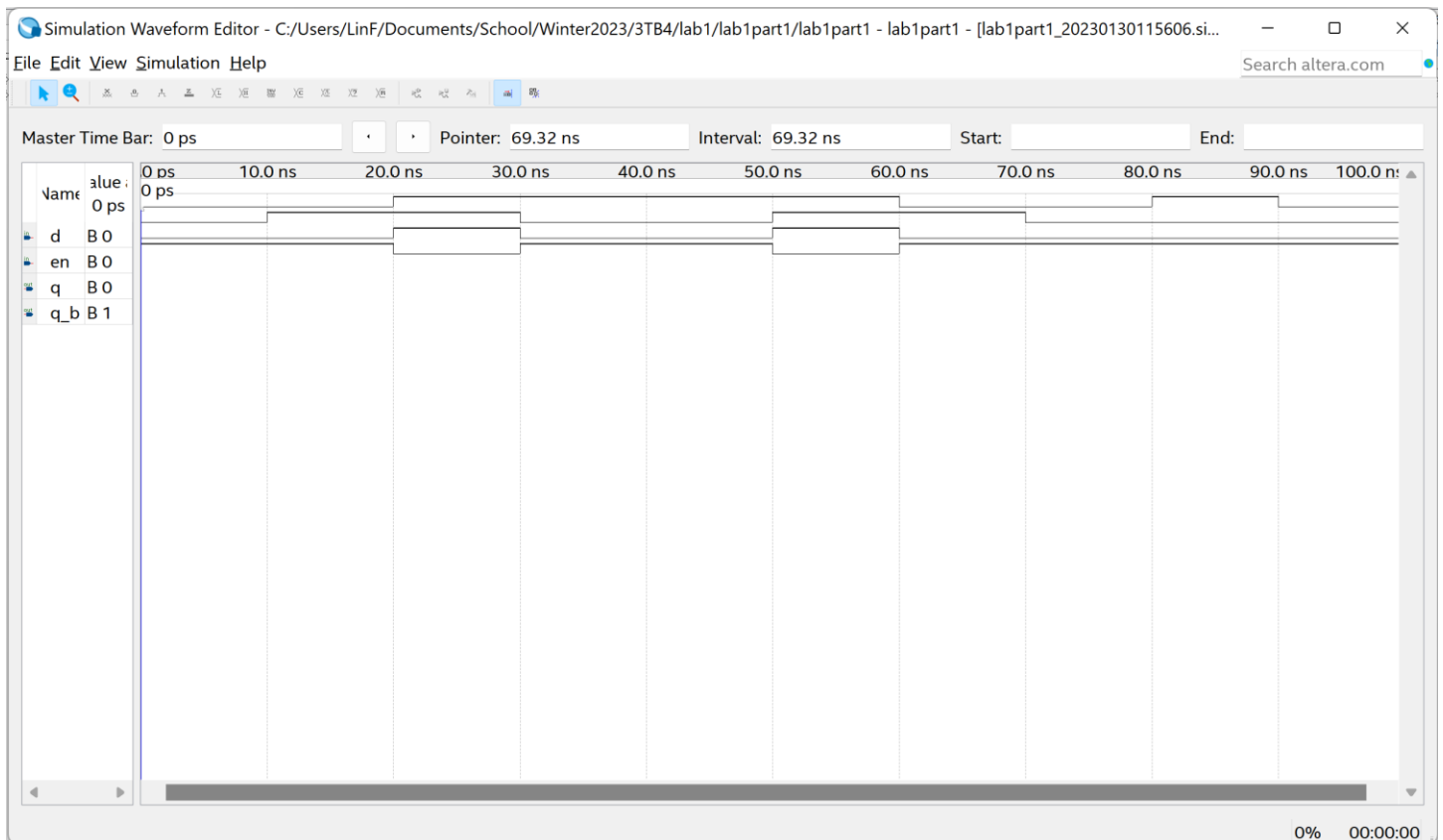


Multiplexer:

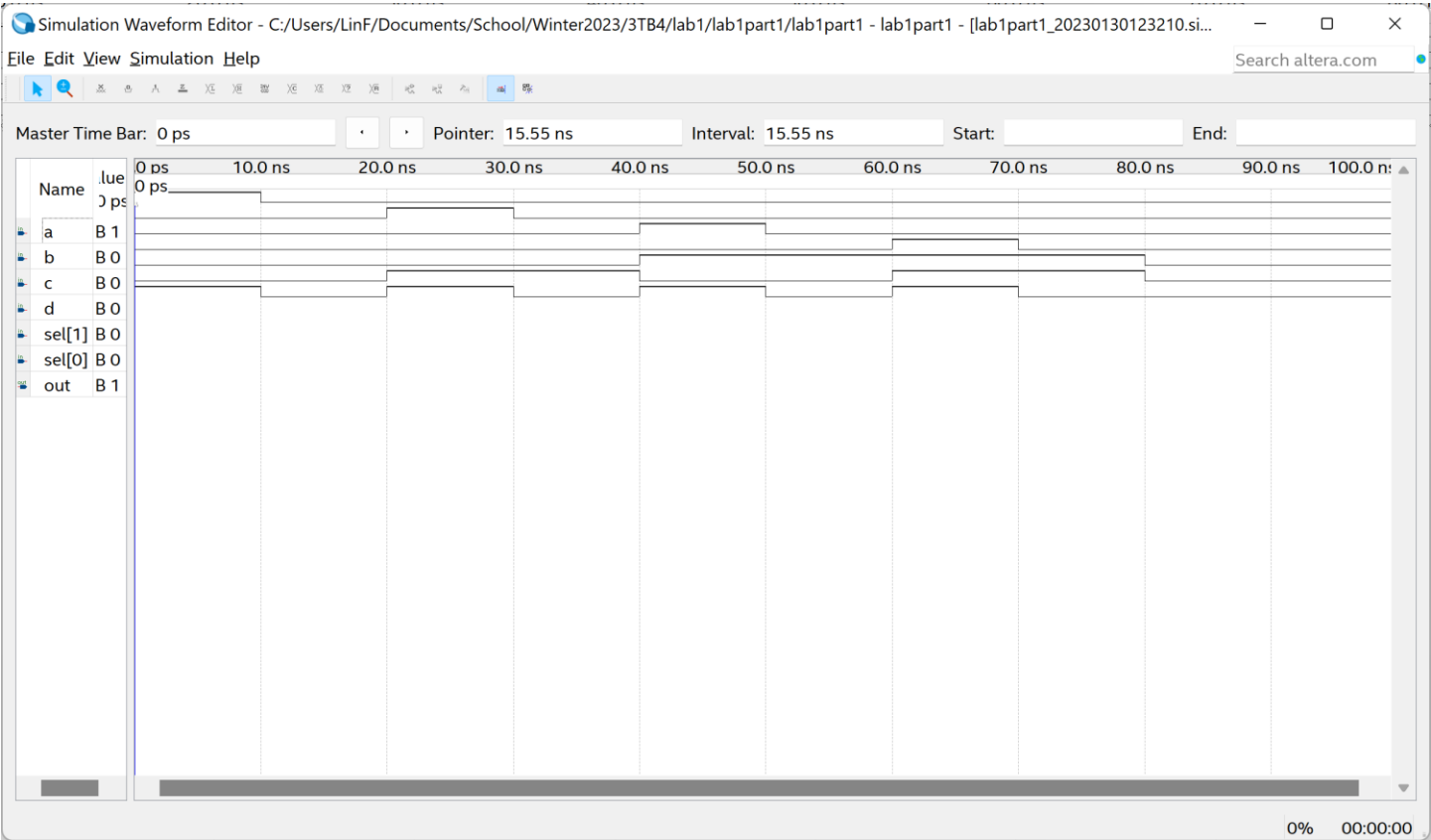

Counter:

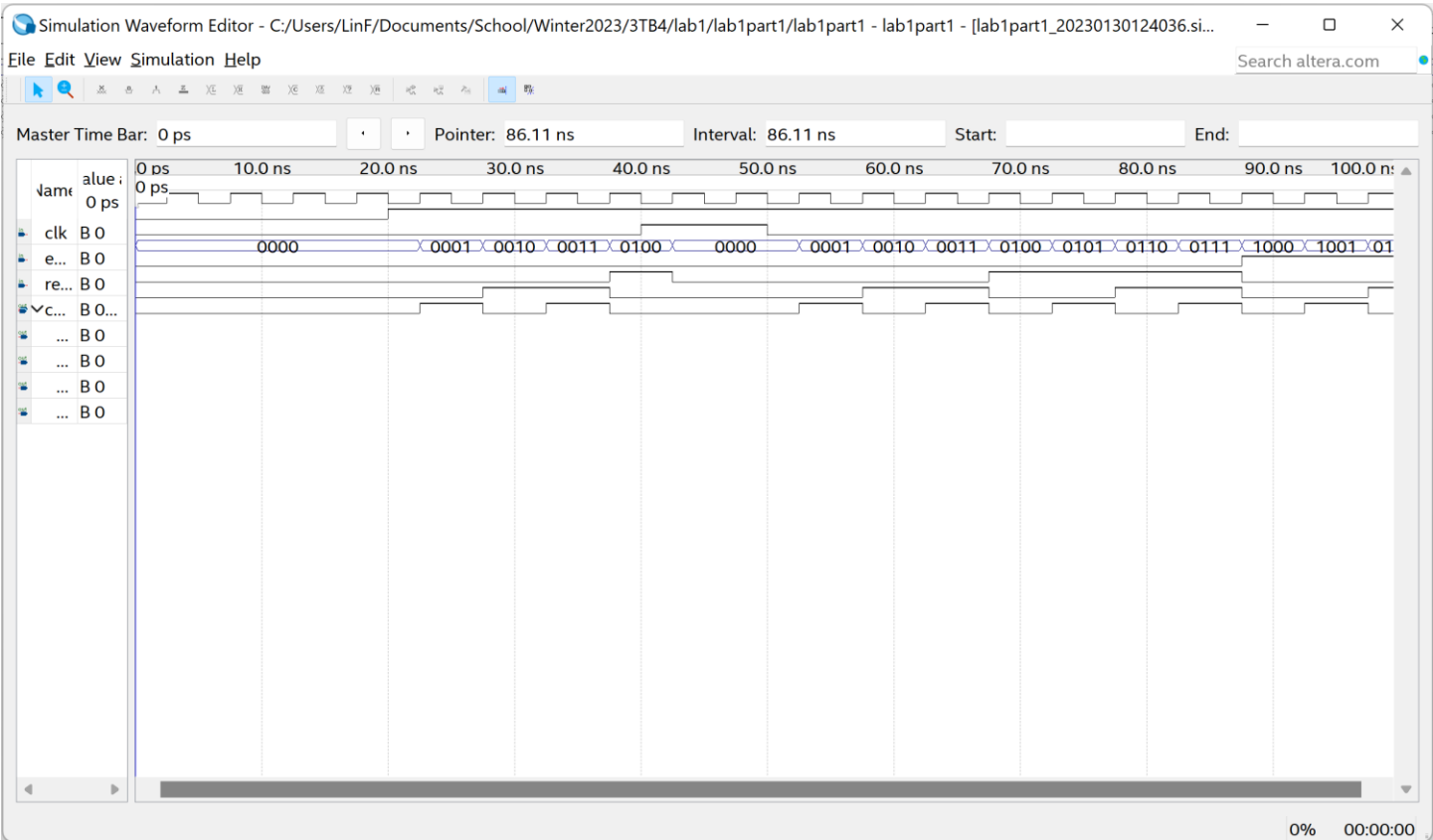


## Lab1part3 RTL view:

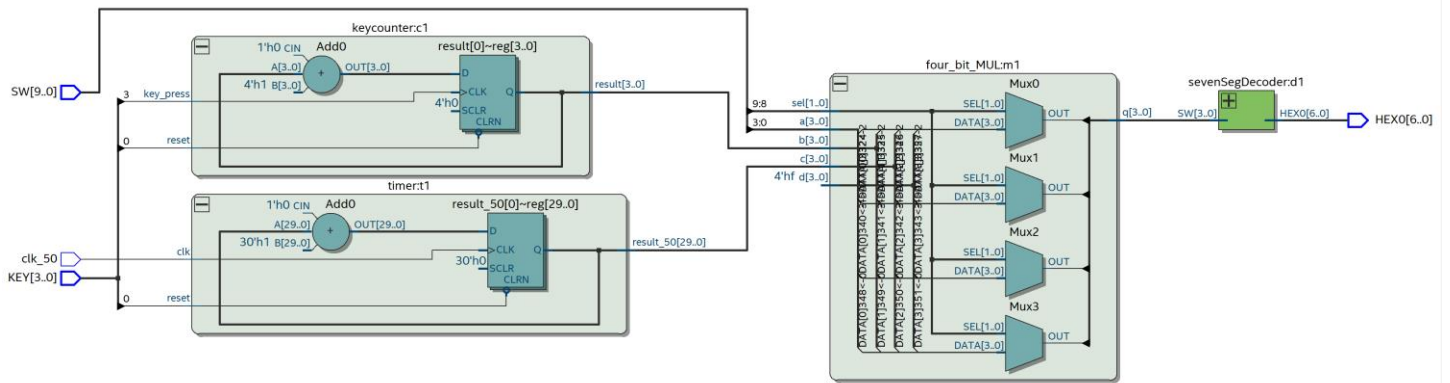

## Lab1part3 Pin Planner:
 
### Top View - Wire Bond Cyclone V - 5CSEMA5F31C6



Node Name	Direction	Location	I/O Bank	VREF Group	Filter Location	I/O Standard	Reserved	Current Strength	Slew Rate	Differential
HEX0[6]	Output	PIN_AH28	5A	B5A_NO	PIN_AH28	2.5 V		12mA ...ault)	1 (default)	
HEX0[5]	Output	PIN_AG28	5A	B5A_NO	PIN_AG28	2.5 V		12mA ...ault)	1 (default)	
HEX0[4]	Output	PIN_AF28	5A	B5A_NO	PIN_AF28	2.5 V		12mA ...ault)	1 (default)	
HEX0[3]	Output	PIN_AG27	5A	B5A_NO	PIN_AG27	2.5 V		12mA ...ault)	1 (default)	
HEX0[2]	Output	PIN_AE28	5A	B5A_NO	PIN_AE28	2.5 V		12mA ...ault)	1 (default)	
HEX0[1]	Output	PIN_AE27	5A	B5A_NO	PIN_AE27	2.5 V		12mA ...ault)	1 (default)	
HEX0[0]	Output	PIN_AE26	5A	B5A_NO	PIN_AE26	2.5 V		12mA ...ault)	1 (default)	
KEY[3]	Input	PIN_Y16	3B	B3B_NO	PIN_Y16	2.5 V		12mA ...ault)		
KEY[2]	Input				PIN_F8	2.5 V ...fault)		12mA ...ault)		
KEY[1]	Input				PIN_AJ16	2.5 V ...fault)		12mA ...ault)		
KEY[0]	Input	PIN_AA14	3B	B3B_NO	PIN_AA14	2.5 V		12mA ...ault)		
SW[9]	Input	PIN_AE12	3A	B3A_NO	PIN_AE12	2.5 V		12mA ...ault)		
SW[8]	Input	PIN_AD10	3A	B3A_NO	PIN_AD10	2.5 V		12mA ...ault)		
SW[7]	Input				PIN_B12	2.5 V ...fault)		12mA ...ault)		
SW[6]	Input				PIN_K8	2.5 V ...fault)		12mA ...ault)		
SW[5]	Input				PIN_H13	2.5 V ...fault)		12mA ...ault)		
SW[4]	Input				PIN_AH29	2.5 V ...fault)		12mA ...ault)		
SW[3]	Input	PIN_AF10	3A	B3A_NO	PIN_AF10	2.5 V		12mA ...ault)		
SW[2]	Input	PIN_AF9	3A	B3A_NO	PIN_AF9	2.5 V		12mA ...ault)		
SW[1]	Input	PIN_AC12	3A	B3A_NO	PIN_AC12	2.5 V		12mA ...ault)		
SW[0]	Input	PIN_AB12	3A	B3A_NO	PIN_AB12	2.5 V		12mA ...ault)		
clk_50	Input	PIN_AF14	3B	B3B_NO	PIN_AF14	2.5 V		12mA ...ault)		
<<new node>>										

## Lab1part3 complication report:

Quartus Prime Lite Edition - C:/Users/Linf/Documents/School/Winter2023/3TB4/lab1/lab1part3/lab1part3 - lab1part3

File Edit View Project Assignments Processing Tools Window Help

lab1part3

Project Navigator Hierarchy lab1part3.v

Entity/Instance

Table of Contents

- Flow Summary
- Flow Settings
- Flow Non-Default Global Settings
- Flow Elapsed Time
- Flow OS Summary
- Flow Log
- Analysis & Synthesis
- Filter
- Flow Messages
- Flow Suppressed Messages
- Assembler
- TimeQuest Timing Analyzer

Flow Summary

Flow Status: Successful - Mon Jan 30 17:07:51 2023

Quartus Prime Version: 17.1.0 Build 590 10/25/2017 SJ Lite Edition

Revision Name: lab1part3

Top-level Entity Name: lab1part3

Family: Cyclone V

Device: 5C5EMA5F31C6

Timing Models: Final

Logic utilization (in ALMs): 24 / 32,070 (< 1 %)

Total registers: 38

Total pins: 22 / 457 (5 %)

Total virtual pins: 0

Total block memory bits: 0 / 4,065,280 (0 %)

Total DSP blocks: 0 / 87 (0 %)

Total HSSI RX PCSs: 0

Total HSSI PMA RX Deserializers: 0

Total HSSI TX PCSs: 0

Total HSSI PMA TX Serializers: 0

Total PLLs: 0 / 6 (0 %)

Total DLLs: 0 / 4 (0 %)

Tasks

Task

- Compile Design
- Analysis & Synthesis
- Filter (Place & Route)
- Assembler (Generate programming files)
- TimeQuest Timing Analysis
- EDA Netlist Writer
- Edit Settings
- Program Device (Open Programmer)

Messages

System (2) Processing (132)

100% 00:00:01

## Answers to lab questions:

1. The DE1-SoC.qsf file includes all the available pin assignments on the DE1-SoC board. By importing this file to the Assignment Editor, it automatically assign pins with names pre-defined in the file, it simplifies the pin assignment process during the lab so we don't have to assign every pin manually.

2.

- Total number of logic elements used by your circuit: 24
- Total number of registers: 38
- Total number of pins: 22
- The maximum number of logic elements that can fit on the FPGA you used: 32,070

## Code for lab1part3:

```
Text Editor - C:/Users/LinF/Documents/School/Winter2023/3TB4/lab1/lab1part3/lab1part3 - lab1part3 - [lab1part3.v]
File Edit View Project Processing Tools Window Help Search altera.com

1 module lab1part3 (input [9:0] SW, input [3:0] KEY, input clk_50, output [6:0] HEX0);
2   reg [6:0] reg_LEDs;
3   wire [3:0] key_counter;
4   wire [3:0] disp_in;
5   wire [6:0] disp_out;
6   wire [29:0] clk_count;
7   wire [3:0] off = 4'b1111;
8   assign HEX0 = disp_out;
9
10  keycounter c1(.reset(KEY[0]), .key_press(KEY[3]), .result(key_counter));
11  timer t1(.clk(clk_50), .reset(KEY[0]), .result_50(clk_count));
12  fourBitMultiplexer m1(.sel(SW[9:8]), .a(SW[3:0]), .b(key_counter), .c(clk_count[29:26]), .d(off), .q(disp_in));
13  sevenSegDecoder d1(.SW(disp_in), .HEX0(disp_out));
14
15 endmodule
16
17 module keycounter(input reset, key_press, output reg[3:0] result);
18   always @(posedge key_press, negedge reset) begin
19     if (!reset) begin
20       result <= 4'b0;
21     end
22     else if (key_press) begin
23       result <= result + 1'b1;
24     end
25     else if (result == 4'b1111 && key_press) begin
26       result <= 4'b0;
27     end
28   end
29 endmodule
30
31 module timer(input clk, reset, output reg[29:0] result_50);
32   always @(posedge clk, negedge reset) begin
33     if (!reset) begin
34       result_50 <= 30'b0;
35     end
36     else begin
37       result_50 <= result_50 + 1'b1;
38     end
39   end
40 endmodule
41
42
43 module fourBitMultiplexer (sel, a, b, c, d, q);
44   input [1:0] sel;
45   input [3:0] a;
46   input [3:0] b;
47   input [3:0] c;
48   input [3:0] d;
49   output reg [3:0] q;
50
51   always @ (sel) begin
52     case (sel)
53       2'b00 : q <= a;
54       2'b01 : q <= b;
55       2'b10 : q <= c;
56       2'b11 : q <= d;
57     endcase
58   end
59 endmodule
60
61
62 module sevenSegDecoder (input [3:0] SW, output [6:0] HEX0);
63   reg [6:0] reg_LEDs;
64
65   assign HEX0[0] = ( (SW[2]&(~SW[1])&(~SW[0])) | ((~SW[3])&(~SW[2])&(~SW[1])&SW[0]) | (SW[3]&SW[1]) );
66   assign HEX0[1] = ( (SW[2]&(~SW[1])&SW[0]) | (SW[3]&SW[2]&SW[0]) | ((~SW[3])&SW[2]&SW[1]&(~SW[0])) | (SW[3]&(~SW[2])&SW[0]) );
67   assign HEX0[6:2] = reg_LEDs[6:2];
68
69   always @(*) begin
70     case (SW)
71       4'b0000 : reg_LEDs[6:2] = 5'b10000; //7'b1000000 decimal 0
72       4'b0001 : reg_LEDs[6:2] = 5'b11110; //7'b1111001 decimal 1
73     endcase
74   end
75 endmodule
```

```

62 module sevenSegDecoder (input [3:0] SW, output [6:0] HEX0);
63     reg [6:0] reg_LEDs;
64
65     assign HEX0[0]= ( (SW[2]&(~SW[1])&(~SW[0])) | ((~SW[3])&(~SW[2])&(~SW[1])&SW[0]) | (SW[3]&SW[1]) );
66     assign HEX0[1]= ( (SW[2]&(~SW[1])&SW[0]) | (SW[3]&SW[2])&SW[0]) | ((~SW[3])&SW[2]&SW[1]&(~SW[0])) | (SW[3]&(~SW[2])&SW[1]&(~SW[0])) );
67     assign HEX0[6:2]=reg_LEDs[6:2];
68
69     always @(*) begin
70         case (SW)
71             4'b0000: reg_LEDs[6:2]=5'b10000; //7'b1000000 decimal 0
72             4'b0001: reg_LEDs[6:2]=5'b11110; //7'b1111001 decimal 1
73             4'b0010: reg_LEDs[6:2]=5'b01001; //7'b0100100 decimal 2
74             4'b0011: reg_LEDs[6:2]=5'b01100; //7'b0110000 decimal 3
75             4'b0100: reg_LEDs[6:2]=5'b00110; //7'b0011001 decimal 4
76             4'b0101: reg_LEDs[6:2]=5'b00100; //7'b0010010 decimal 5
77             4'b0110: reg_LEDs[6:2]=5'b00000; //7'b0000010 decimal 6
78             4'b0111: reg_LEDs[6:2]=5'b11110; //7'b1111000 decimal 7
79             4'b1000: reg_LEDs[6:2]=5'b00000; //7'b0000000 decimal 8
80             4'b1001: reg_LEDs[6:2]=5'b00100; //7'b0010000 decimal 9
81             4'b1010: reg_LEDs[6:2]=5'b10001; //7'b1000111 letter L
82             4'b1011: reg_LEDs[6:2]=5'b11110; //7'b1111001 letter I
83             4'b1100: reg_LEDs[6:2]=5'b10010; //7'b1001001 letter N
84             4'b1101: reg_LEDs[6:2]=5'b00011; //7'b0001110 letter F
85             4'b1110: reg_LEDs[6:2]=5'b10000; //7'b1000001 letter U
86             4'b1111: reg_LEDs[6:2]=5'b11111; //7'b1111111 OFF
87             /* finish the case block */
88             default: reg_LEDs[6:2] = 5'bx;
89         endcase
90     end
91 endmodule
92

```