


3TB4 Tutorial/Prelab 1 Report

Lin Fu ful10 400234794


Keyin Liang liangk10 400236736

Quartus Prime Introduction Using Verilog Designs:

Compilation Report:

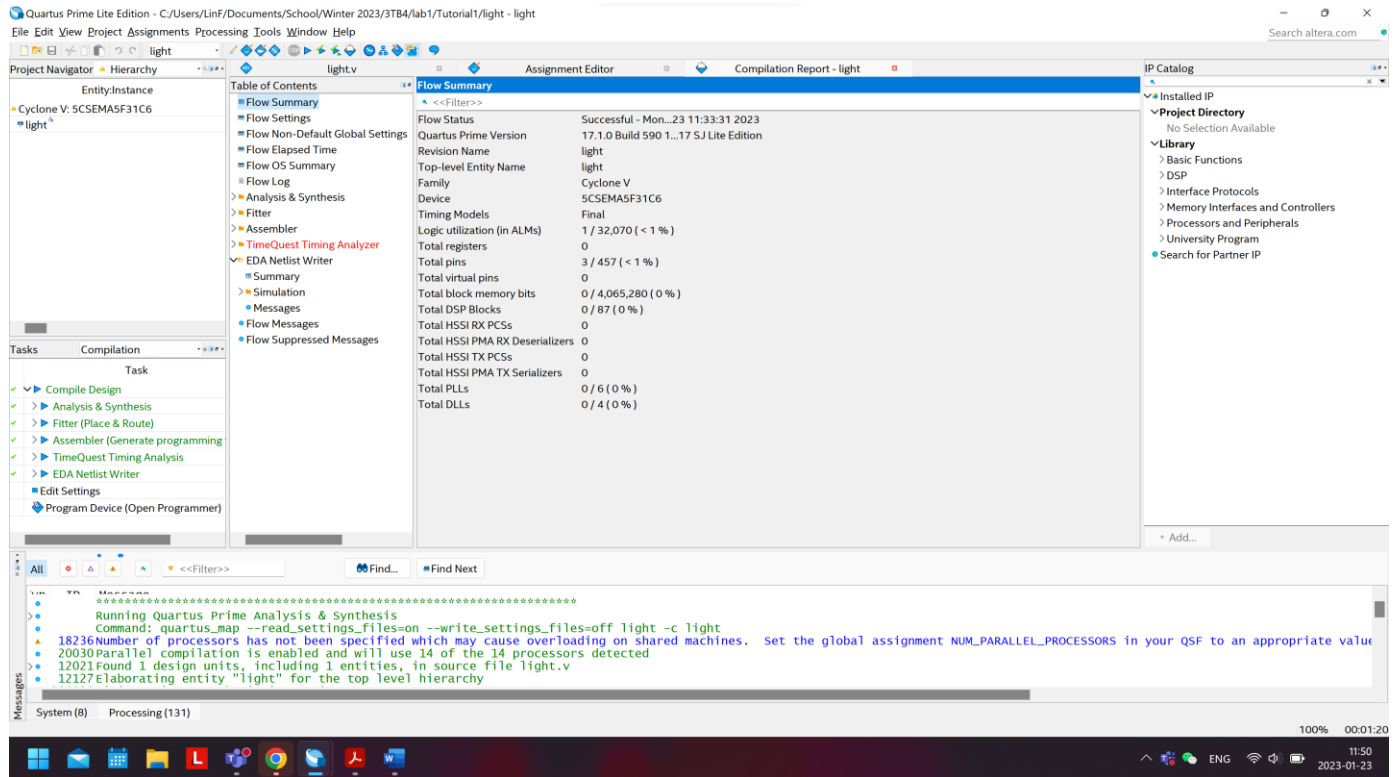


Simulation Report:

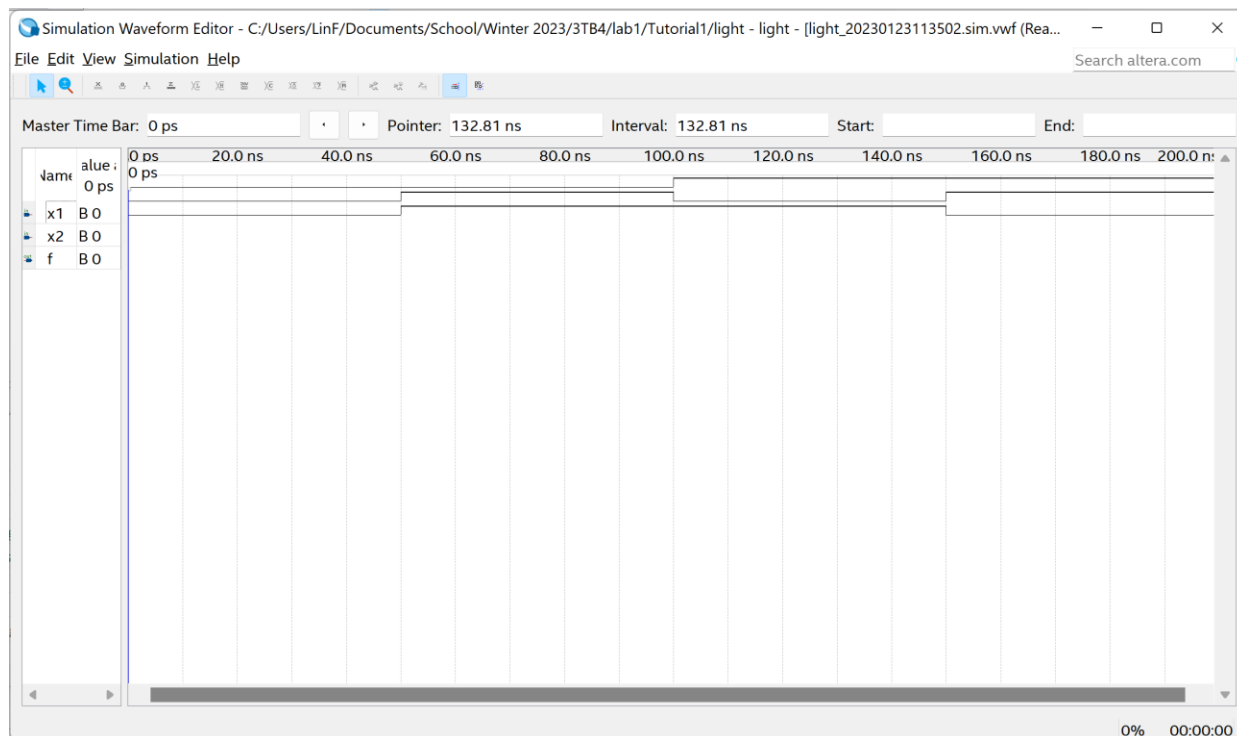


Introduction to Simulation of Verilog Designs:

Simulation Report:

 

Simulation Report Modified:

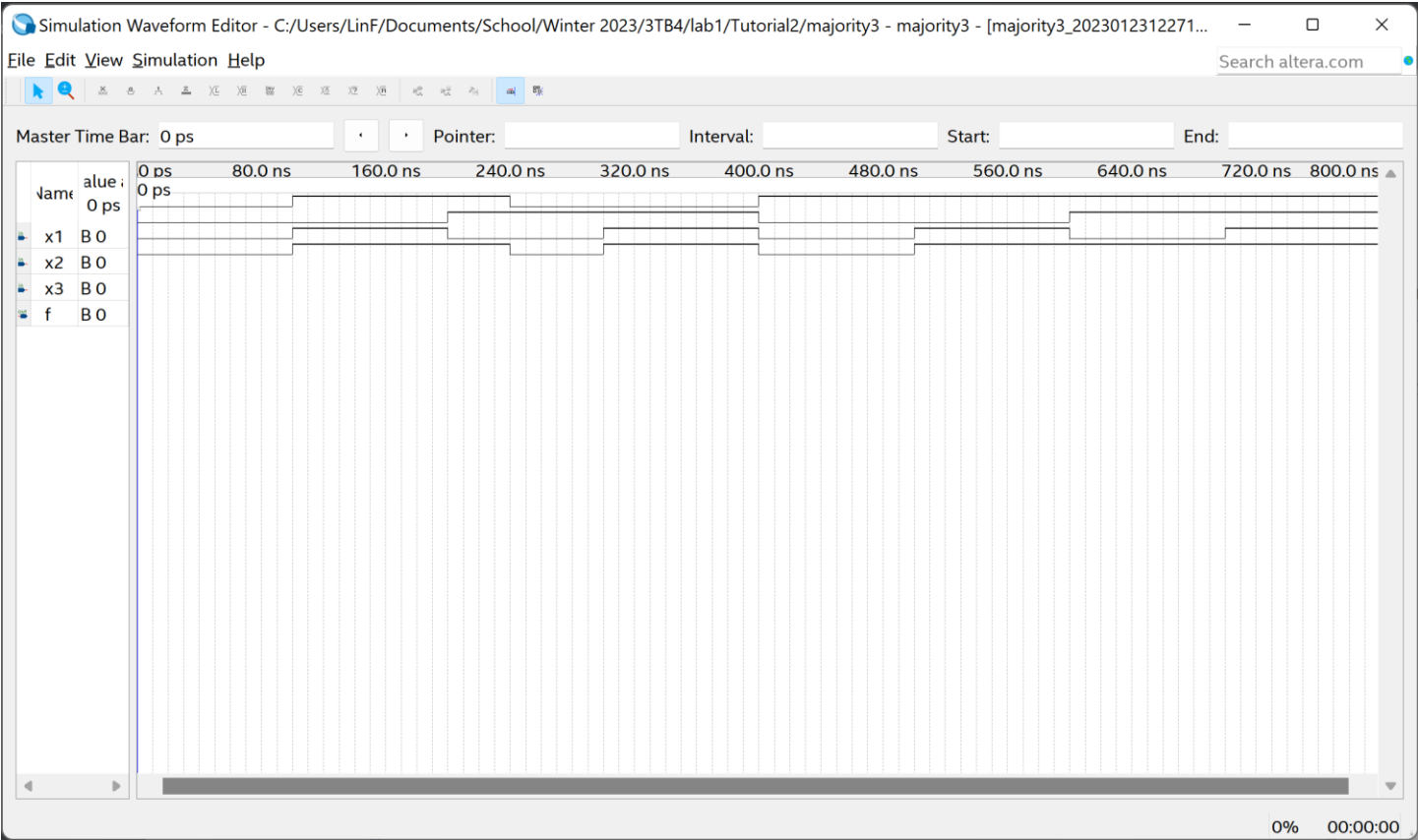

Compilation Report:

Quartus Prime Lite Edition - C:/Users/LinF/Documents/School/Winter 2023/3TB4/lab1/Tutorial2/majority3 - majority3

File Edit View Project Assignments Processing Tools Window Help

majority3

Project Navigator Hierarchy Entity: Instance Cyclone V: 5CSEMA5F31C6 majority3

Table of Contents

- Flow Summary
- Flow Settings
- Flow Non-Default Global Settings
- Flow Elapsed Time
- Flow OS Summary
- Flow Log
- Analysis & Synthesis
- Fitter
- Flow Messages
- Flow Suppressed Messages
- Assembler
- TimeQuest Timing Analyzer

Flow Summary

Flow Status: Successful - Mon...23 12:09:47 2023

Quartus Prime Version: 17.1.0 Build 590 1...17 S.J Lite Edition

Revision Name: majority3

Top-level Entity Name: majority3

Family: Cyclone V

Device: 5CSEMA5F31C6

Timing Models: Final

Logic utilization (in ALMs): 1 / 32,070 (< 1 %)

Total registers: 0

Total pins: 4 / 457 (< 1 %)

Total virtual pins: 0

Total block memory bits: 0 / 4,065,280 (0 %)

Total DSP Blocks: 0 / 87 (0 %)

Total HSSI RX PCSs: 0

Total HSSI PMA RX Deserializers: 0

Total HSSI TX PCSs: 0

Total HSSI PMA TX Serializers: 0

Total PLLs: 0 / 6 (0 %)

Total DLLs: 0 / 4 (0 %)

Tasks Compilation

Task

- Compile Design
- Analysis & Synthesis
- Fitter (Place & Route)
- Assembler (Generate programming)
- TimeQuest Timing Analysis
- EDA Netlist Writer
- Edit Settings
- Program Device (Open Programmer)

Messages

System (6) Processing (125)

100% 00:01:48

12:34 2023-01-23

Prelab Questions:

1. What is the reg data type and what is the wire data type in Verilog?

The reg data type is the hardware registers that stores data, the wire data type describes the connection between elements or hardware entities.

2. Can the wire data type be used on the left side of the assignment statement in a procedural block?

No, the wire data type can only be used on the left side when outside of the procedural block (always block).

3. What are the rules for module port connection?

First, declare input, inout or output as: input/output/inout [range_val:range_var] list_of_identifiers; Inputs are type net and can be connected to a variable of type reg or net. Outputs are type net or reg and must be connected to a variable of type net. Inouts are type net and can only be connected to a variable net type.

4. What are continuous assignment, blocking assignment and nonblocking assignment?

Continuous assignment: Assign values to the nets (LHS) whenever there is a change on the RHS.

Blocking assignment: Blocking the next execution until the current statement is executed. The statements are executed in order.

Nonblocking assignments: Simultaneously execute statements.

5. What is the difference in procedural coding when implementing combinational logic and sequential logic?

Combinational logic does not require a clock to operate, whereas sequential logic does.

6. How does one avoid inferred latches when using Verilog to describe circuits?

To avoid this, make sure that all of the if statements that are used in combinational always blocks have one last else statement to catch all missing conditions.

Always make sure every variable in the procedural block gets assigned.

Use default assignments at the beginning of the procedure, so that every signal is assigned.

7. What is the difference between the operators "<<" and "<<<"?

"<<<" is the arithmetic left shift and "<<" is a logical shift. They both shift left specific bits while "<<" fills the vacated bits with 0, "<<<" fills the vacated bit positions with the value of the sign bit if the expression is signed, otherwise fills with 0.

8. How to declare an array of 6 elements of a 7-bit wire?

Wire[6:0] array[5:0]

One bit data width D flipflop:

```
module D_flipflop (input d, clk, output reg q, output q_b);
    always @(posedge clk) begin
        q <= d;
    end
    assign q_b = ~q;
endmodule
```

One bit data width D flip-flop with active low synchronous reset:

```
module D_ffwActiveLowSyncReset (input d, clk, reset, output reg q, output q_b);
    always @(posedge clk) begin
        if (~reset) begin
            q <= 1'b0;
        end
        else begin
            q <= d;
        end
    end
    assign q_b = ~q;
endmodule
```

One bit data width D flip-flop with active low synchronous reset and active low enable:

```
module D_ffwALSR_ALenable (input d, clk, reset, enable, output reg q, q_b);
    always @(posedge clk) begin
        if (~enable) begin
            if (reset == 1'b0) begin
                q = 1'b0;
            end
            q <= d;
        end
    end
    assign q_b = ~q;
endmodule
```

```
module D_latch (input d, en, output reg q, q_b);
    always @(*) begin
        if (en) begin
            q <= d;
        end
    end
    assign q_b = ~q;
endmodule
```

```
module multiplexer (input a, b, c, d, s1, s2, output reg out);
    always @(*) begin
        case (s1 | s2)
            2'b00: out <= a;
            2'b01: out <= b;
            2'b10: out <= c;
            2'b11: out <= d;
        endcase
    end
endmodule
```

```
module counter (input reset, enable, output reg [3:0]count);
    always @(posedge) begin
        if (enable) begin
            count <= count + 1'b1;
            if (reset) begin
                count <= 4'b0;
            end
            else if (count == 4'b1111) begin
                count <= 4'b0;
            end
        end
    end
endmodule
```

[illegible]

K-map for segment 0 and 1

Segment 0

AB\CD	00	01	11	10
00	0	1	0	0
01	1	0	0	0
11	1	0	1	1
10	0	0	1	1

Segment 1

AB\CD	00	01	11	10
00	0	0	0	0
01	0	1	0	1
11	0	1	1	0
10	0	0	0	1

$$\text{Segment 0 logic} = B\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + AC$$

$$\text{Segment 1 logic} = B\bar{C}D + ABD + \bar{A}BC\bar{D} + \bar{A}\bar{B}C\bar{D}$$

```

module seven_seg_decoder(input [3:0] x, output [6:0] hex_LEDs);
    reg [6:0] reg_LEDs;

    assign hex_LEDs[0] = ( (x[2]&(~x[1])&(~x[0])) | ((~x[3])&(~x[2])&(~x[1])&x[0]) | (x[3]&x[1]) );
    assign hex_LEDs[1] = ( (x[2]&(~x[1])&x[0]) | (x[3]&x[2]&x[0]) | ((~x[3])&x[2]&x[1]&(~x[0])) | (x[3]&(~x[2])&x[1]&(~x[0])) );
    assign hex_LEDs[6:2]=reg_LEDs[6:2];

    always @(*) begin
        case (x)
            4'b0000: reg_LEDs[6:2]=5'b10000; //7'b1000000 decimal 0
            4'b0001: reg_LEDs[6:2]=5'b11110; //7'b1111001 decimal 1
            4'b0010: reg_LEDs[6:2]=5'b01001; //7'b0100100 decimal 2
            4'b0011: reg_LEDs[6:2]=5'b01100; //7'b0110000 decimal 3
            4'b0100: reg_LEDs[6:2]=5'b00110; //7'b0011001 decimal 4
            4'b0101: reg_LEDs[6:2]=5'b00100; //7'b0010010 decimal 5
            4'b0110: reg_LEDs[6:2]=5'b00000; //7'b0000010 decimal 6
            4'b0111: reg_LEDs[6:2]=5'b11110; //7'b1111000 decimal 7
            4'b1000: reg_LEDs[6:2]=5'b00000; //7'b0000000 decimal 8
            4'b1001: reg_LEDs[6:2]=5'b00100; //7'b0010000 decimal 9
            4'b1010: reg_LEDs[6:2]=5'b10001; //7'b1000111 letter L
            4'b1011: reg_LEDs[6:2]=5'b11110; //7'b1111001 letter I
            4'b1100: reg_LEDs[6:2]=5'b00110; //7'b0011001 letter N
            4'b1101: reg_LEDs[6:2]=5'b00011; //7'b0001110 letter F
            4'b1110: reg_LEDs[6:2]=5'b10000; //7'b1000001 letter U
            4'b1111: reg_LEDs[6:2]=5'b11111; //7'b1111111 OFF
            /* finish the case block */
            default: reg_LEDs[6:2] = 5'bx;
        endcase
    end
endmodule

```